


HY220

Εργαστήριο Ψηφιακών Κυκλωμάτων

Χειμερινό Εξάμηνο
2017-2018

Δυναμικές Μνήμες - DRAM


 
Βασικό Block Diagram Υποσυστημάτων Μνήμης



RAM/ROM ονοματολογία:


32 X 8, "32 by 8" => 32 8-bit words

1M X 1, "1 meg by 1" => 1M 1-bit words

  


Κελί μνήμης με 1 transistor (DRAM)


- **Εγγραφή - Write:**
 1. Οδηγούμε την bit line
 2. Επιλέγουμε γραμμή (row select)
- **Ανάγνωση - Read:**
 1. Προφορτίζουμε (precharge) την bit line σε $V_{dd}/2$
 2. Επιλέγουμε γραμμή (row select)
 3. Το κελί και η bit line μοιράζονται τα φορτία (charge sharing)
 4. Sense στην bit line (sense amplifier)
Μπορεί να ανιχνεύει πολύ μικρές αλλαγές
 5. Write: επαναφέρουμε την τιμή
- **Ανανέωση - Refresh :**
 - Αρκεί ένα απλό read σε κάθε κελί

 

Κλασική Οργάνωση DRAM (τετραγωνική)

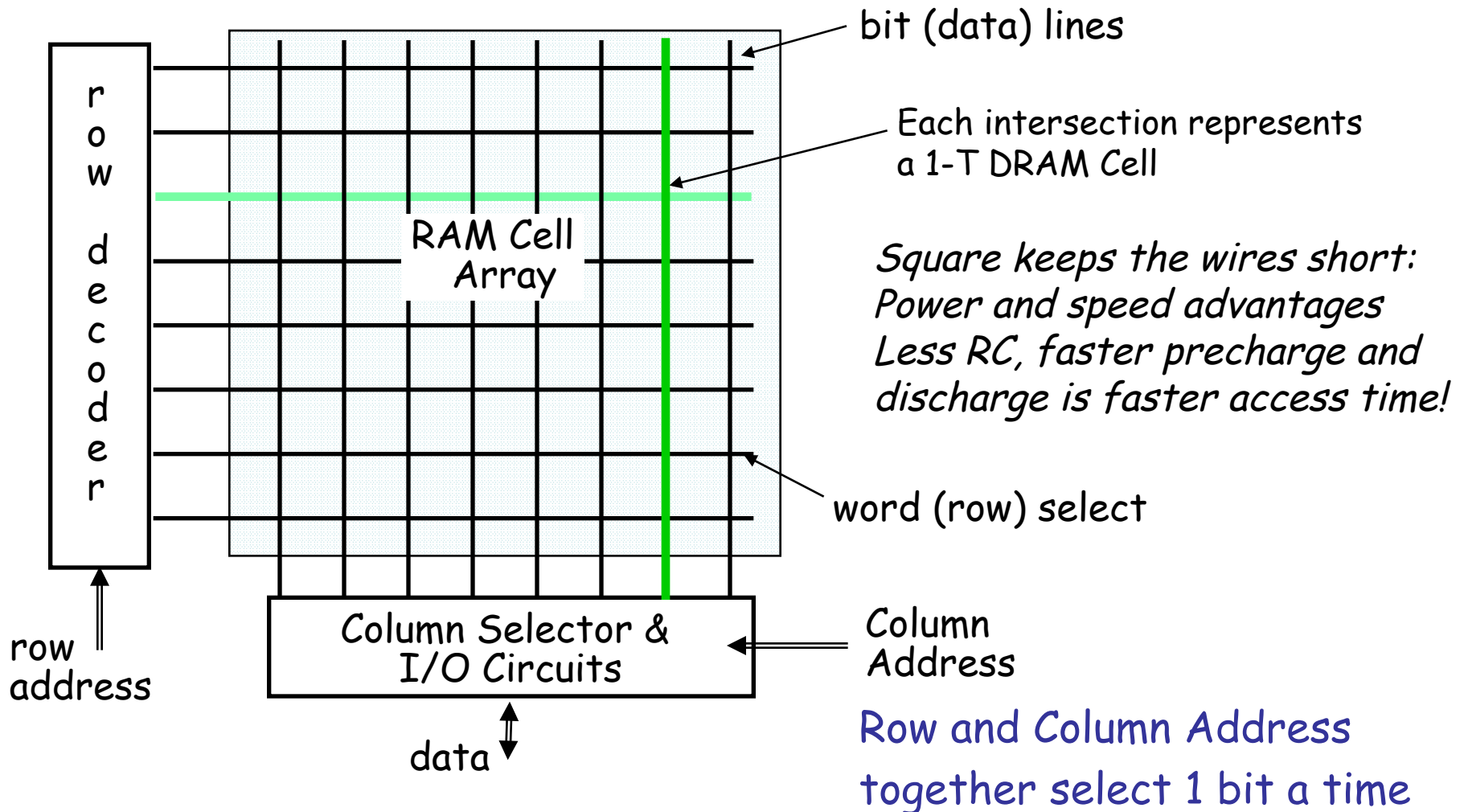


Λογική Οργάνωση DRAM (4 Mbit)

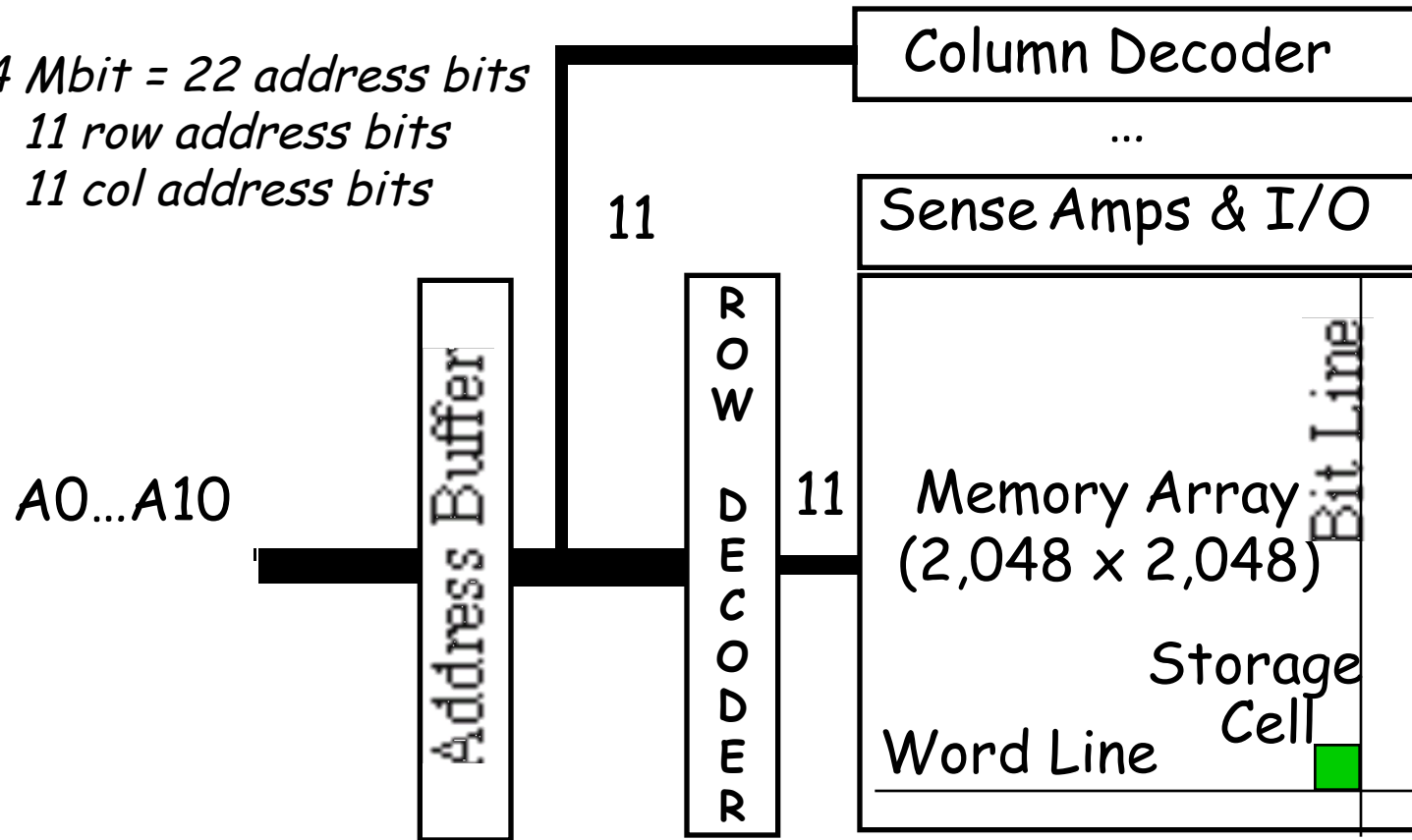

- Square root of bits per RAS/CAS
 - Row selects 1 row of 2048 bits from 2048 rows
 - Col selects 1 bit out of 2048 bits in such a row


Τα σήματα της DRAM

 


- Σήματα ελέγχου (RAS_L, CAS_L, WE_L, OE_L) όλα active low
- Κοινό bus δεδομένων D - εισόδου και εξόδου (Din & Dout):
 - WE_L ενεργοποιείται (Low), OE_L απενεργοποιείται (High)
 - D χρησιμοποιείται σαν είσοδος στην DRAM
 - WE_L απενεργοποιείται (High), OE_L ενεργοποιείται (Low)
 - D χρησιμοποιείται σαν έξοδος από την DRAM
- Οι διευθύνσεις γραμμής και στήλης μοιράζονται τα ίδια pins (A)
 - RAS_L ενεργοποιείται (low) -> A αποθηκεύεται σαν row address
 - CAS_L ενεργοποιείται (low) -> A αποθηκεύεται σαν column address
 - RAS/CAS edge-sensitive

Απλοποιημένο διάγραμμα χρονισμού DRAM

Read

 

Write


 


- Η διεύθυνση δίνεται σε 2 βήματα

Τυπικός χρονοισμός Ανάγνωσης DRAM

• Κάθε προσπέλαση DRAM ξεκινάει με:

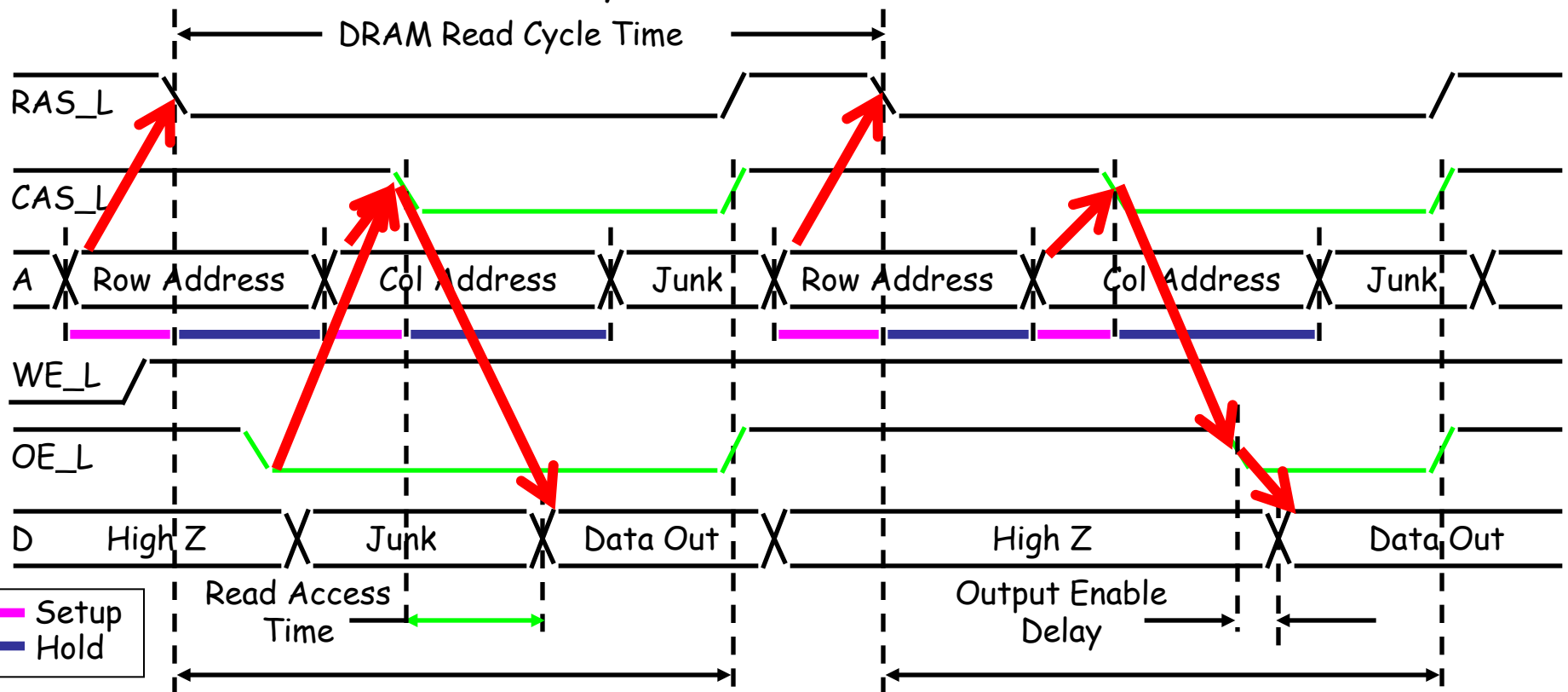 - Ενεργοποίηση του RAS_L
- 2 τρόποι ανάγνωση: early or late



Early Read Cycle: OE_L asserted before CAS_L

Late Read Cycle: OE_L asserted after CAS_L

Τα βήματα για Early Read



- Assert Row Address
- Assert RAS_L
 - Start read cycle
 - Meet Row Addr setup time before RAS/hold time after RAS
- Assert OE_L
- Assert Col Address
- Assert CAS_L
 - Meet Col Addr setup time before CAS/hold time after CAS
- Valid Data Out after access time
- Disassert OE_L, CAS_L, RAS_L to end cycle

Τα βήματα για Late Read

- Assert Row Address
- Assert RAS_L
 - Start read cycle
 - Meet Row Addr setup time before RAS/hold time after RAS
- Assert Col Address
- Assert CAS_L
 - Meet Col Addr setup time before CAS/hold time after CAS
- Assert OE_L
- Valid Data Out after access time
- Disassert OE_L, CAS_L, RAS_L to end cycle

Τυπικός χρονοσμός Εγγραφής DRAM

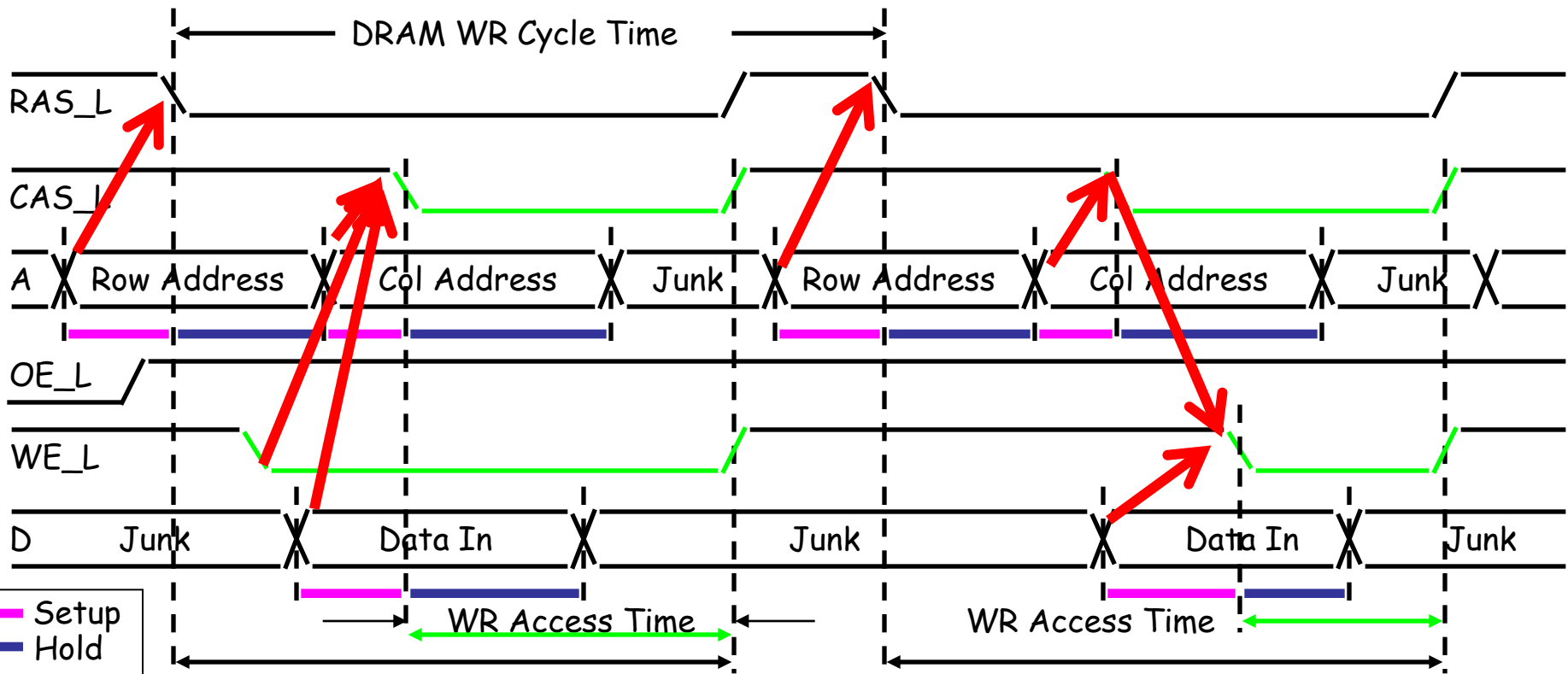 - Κάθε προσπέλαση DRAM ξεκινάει με:
 - Ενεργοποίηση του RAS_L
 - 2 τρόποι εγγραφής: early or late




Early Wr Cycle: WE_L asserted before CAS_L

Late Wr Cycle: WE_L asserted after CAS_L

Key DRAM Timing Parameters

- t_{RAC} : minimum time from RAS line falling to the valid data output.
 - Quoted as the speed of a DRAM
 - A fast 4Mb DRAM $t_{RAC} = 60$ ns
- t_{RC} : minimum time from the start of one row access to the start of the next.
 - $t_{RC} = 110$ ns for a 4Mbit DRAM with a t_{RAC} of 60 ns
- t_{CAC} : minimum time from CAS line falling to valid data output.
 - 15 ns for a 4Mbit DRAM with a t_{RAC} of 60 ns
- t_{PC} : minimum time from the start of one column access to the start of the next.
 - 35 ns for a 4Mbit DRAM with a t_{RAC} of 60 ns

DRAM with Column buffer

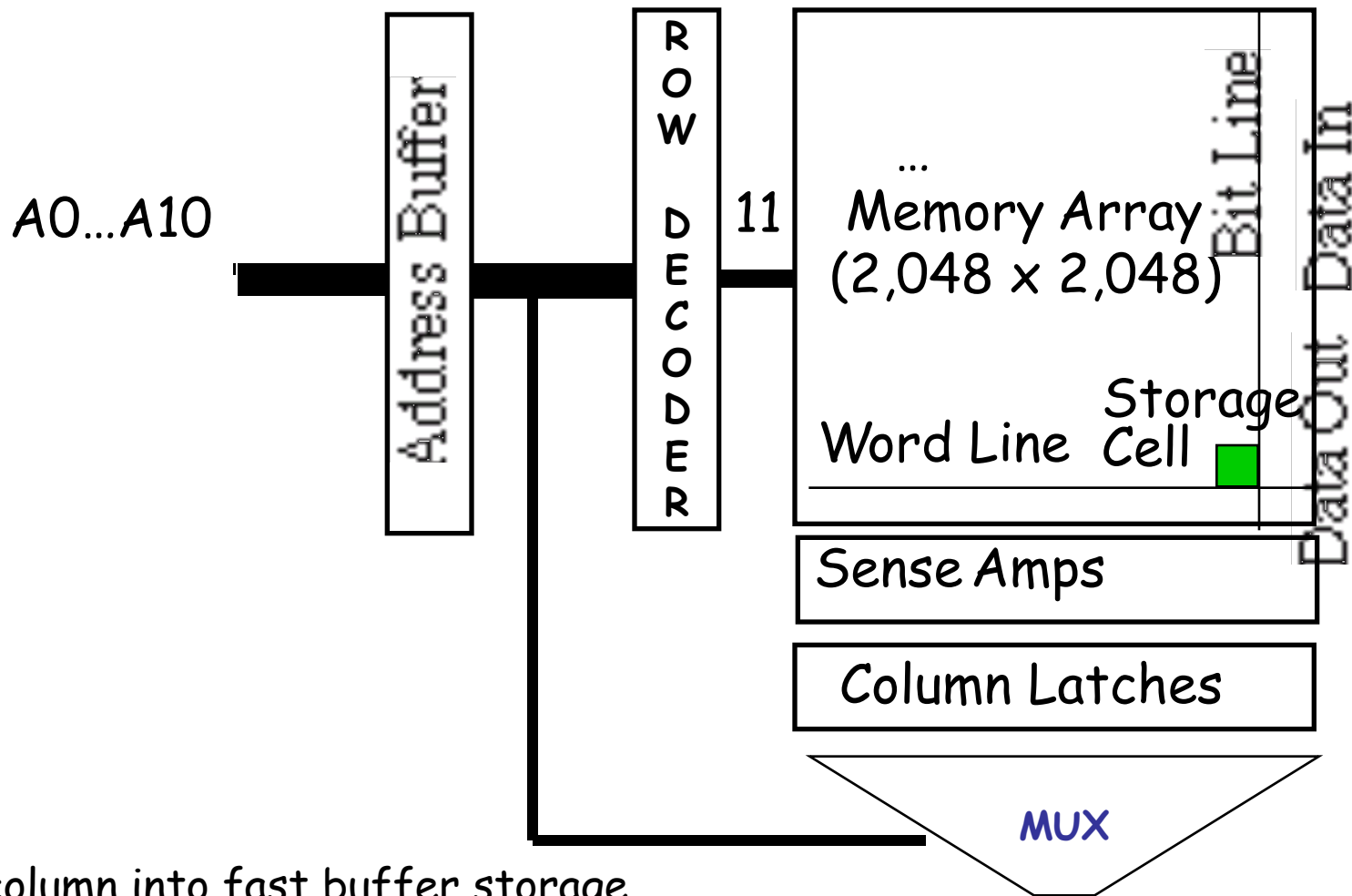


Pull column into fast buffer storage

Access sequence of bit from there

Optimized Access to Cols in Row


- Often want to access a sequence of bits
- Page mode
 - After RAS / CAS, can access additional bits in the row by changing column address and strobing CAS
- Static Column mode
 - Change column address (without repeated CAS) to get different bit
- Nibble mode
 - Pulsing CAS gives next bit mod 4
- Video ram
 - Serial access

256 Mbit SDRAM Addressing

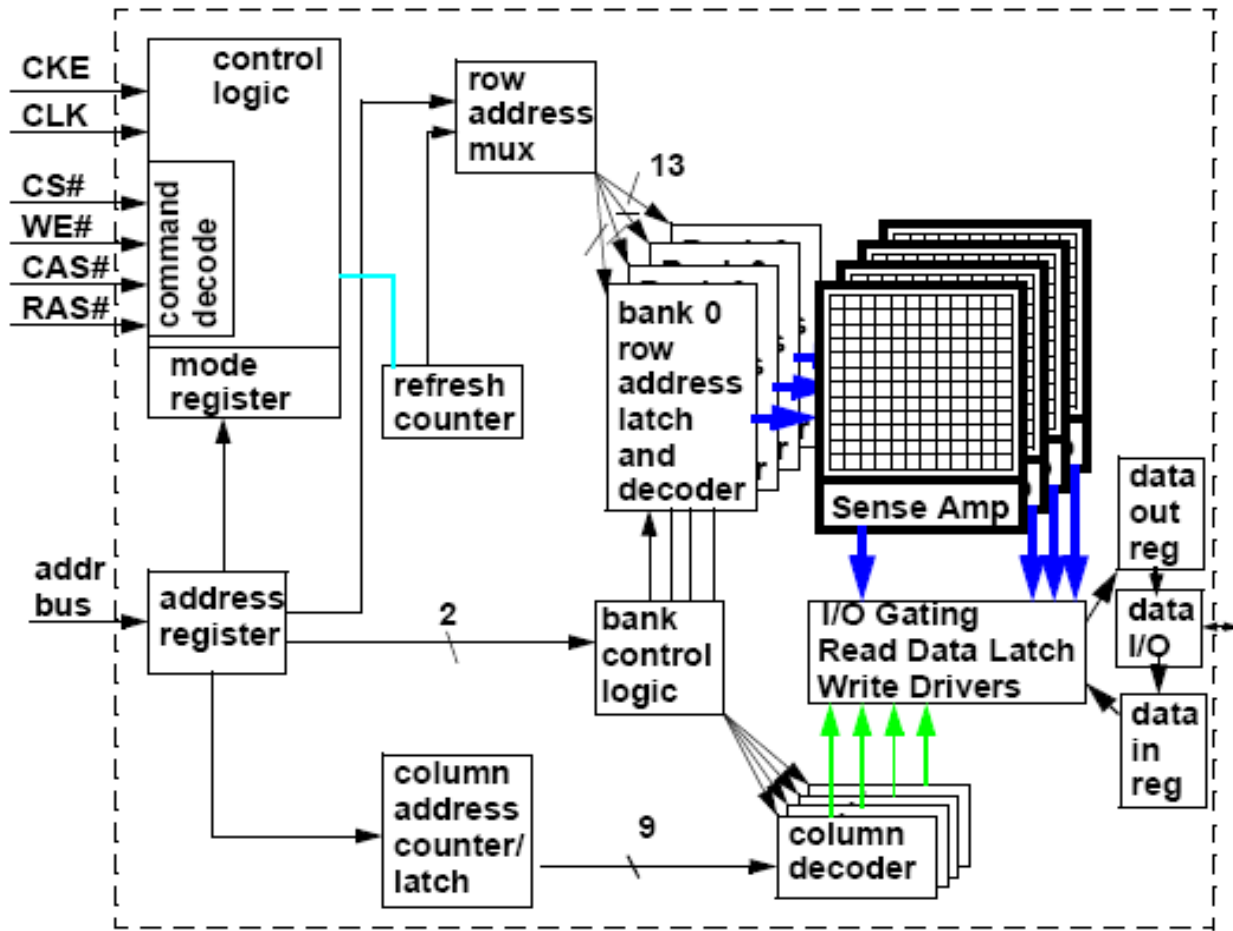

256 Mbit chip: 8192 rows, 512 columns, x16 data, 4 banks

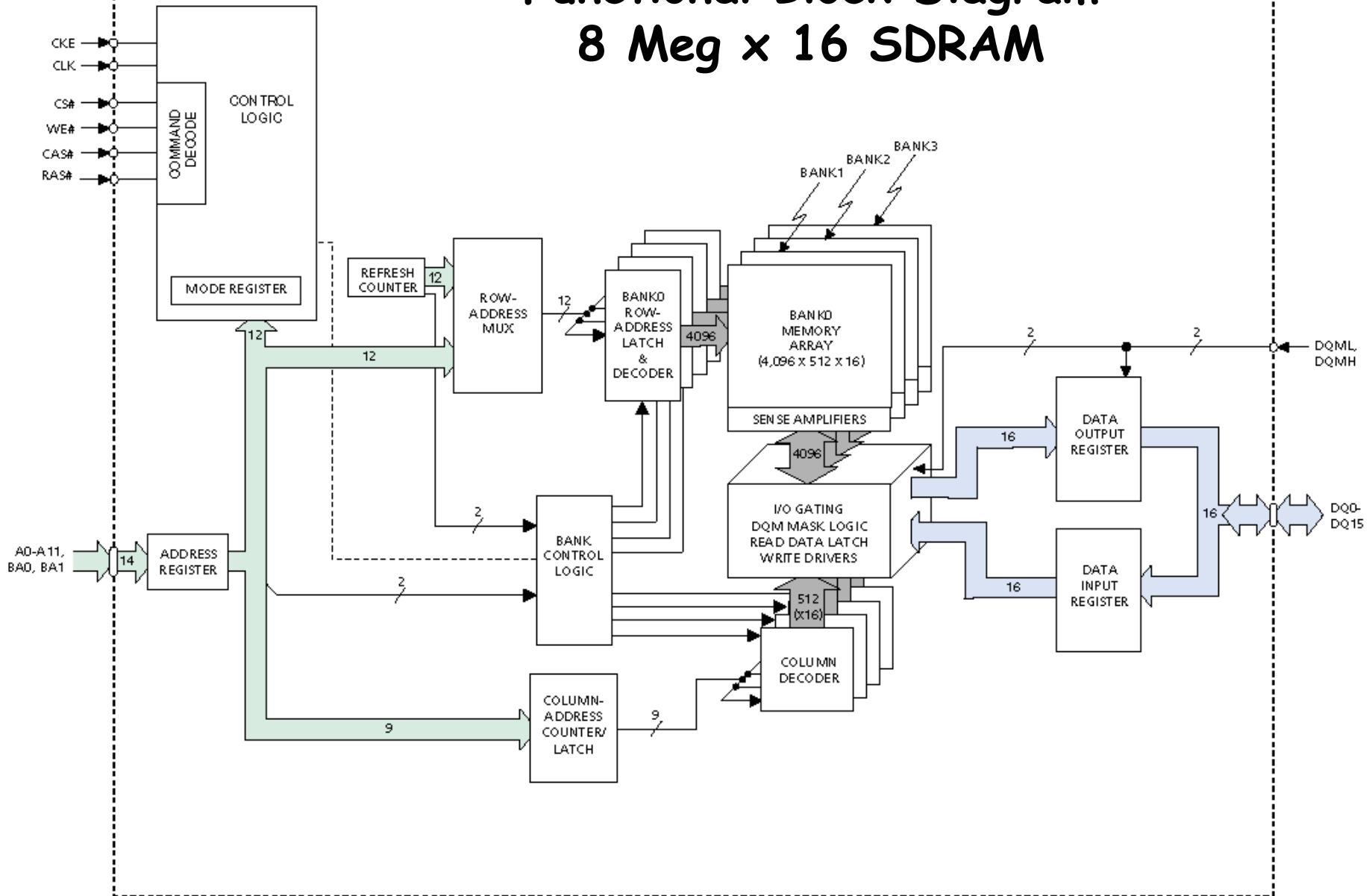
Functional Block Diagram 8 Meg x 16 SDRAM



SDRAM Details

- Multiple "banks" of cell arrays are used to reduce access time:
 - Each bank is 4K rows by 512 "columns" by 16 bits (for our part)
- Read and Write operations are split into RAS (row access) followed by CAS (column access)
- These operations are controlled by sending commands
 - Commands are sent using the RAS, CAS, CS, & WE pins.
- Address pins are "time multiplexed"
 - During RAS operation, address lines select the bank and row
 - During CAS operation, address lines select the column.
- "ACTIVE" command "opens" a row for operation
 - transfers the contents of the entire row to a row buffer
- Subsequent "READ" or "WRITE" commands modify the contents of the row buffer.
- For burst reads and writes during "READ" or "WRITE" the starting address of the block is supplied.
 - Burst length is programmable as 1, 2, 4, 8 or a "full page" (entire row) with a burst terminate option.
- Special commands are used for initialization (burst options etc.)
- A burst operation takes $\approx 4 + n$ cycles (for n words)

Mode Register

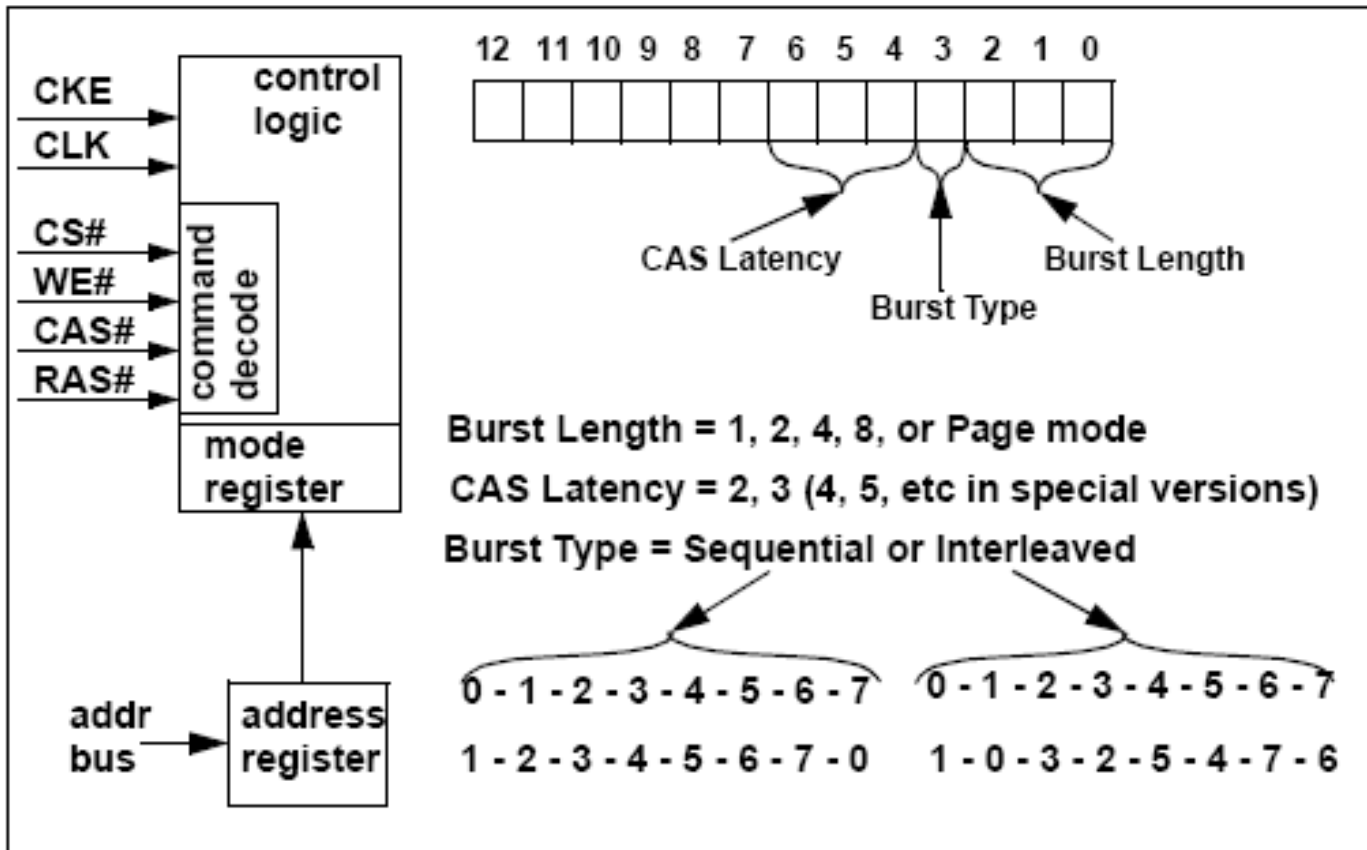


SDRAM Device can be programmed to respond in slightly different manners


Βασικές Χρονικές Παράμετροι SDRAM

- t_{RCD} : ACTIVE to READ or WRITE delay
- CL : CAS Latency
- t_{RAS} : ACTIVE to PRECHARGE time
- t_{RP} : PRECHARGE Period
- t_{WR} : WRITE recovery time
- t_{RC} : ACTIVE to ACTIVE time


READ burst (with auto precharge)

 


WRITE burst (with auto precharge)

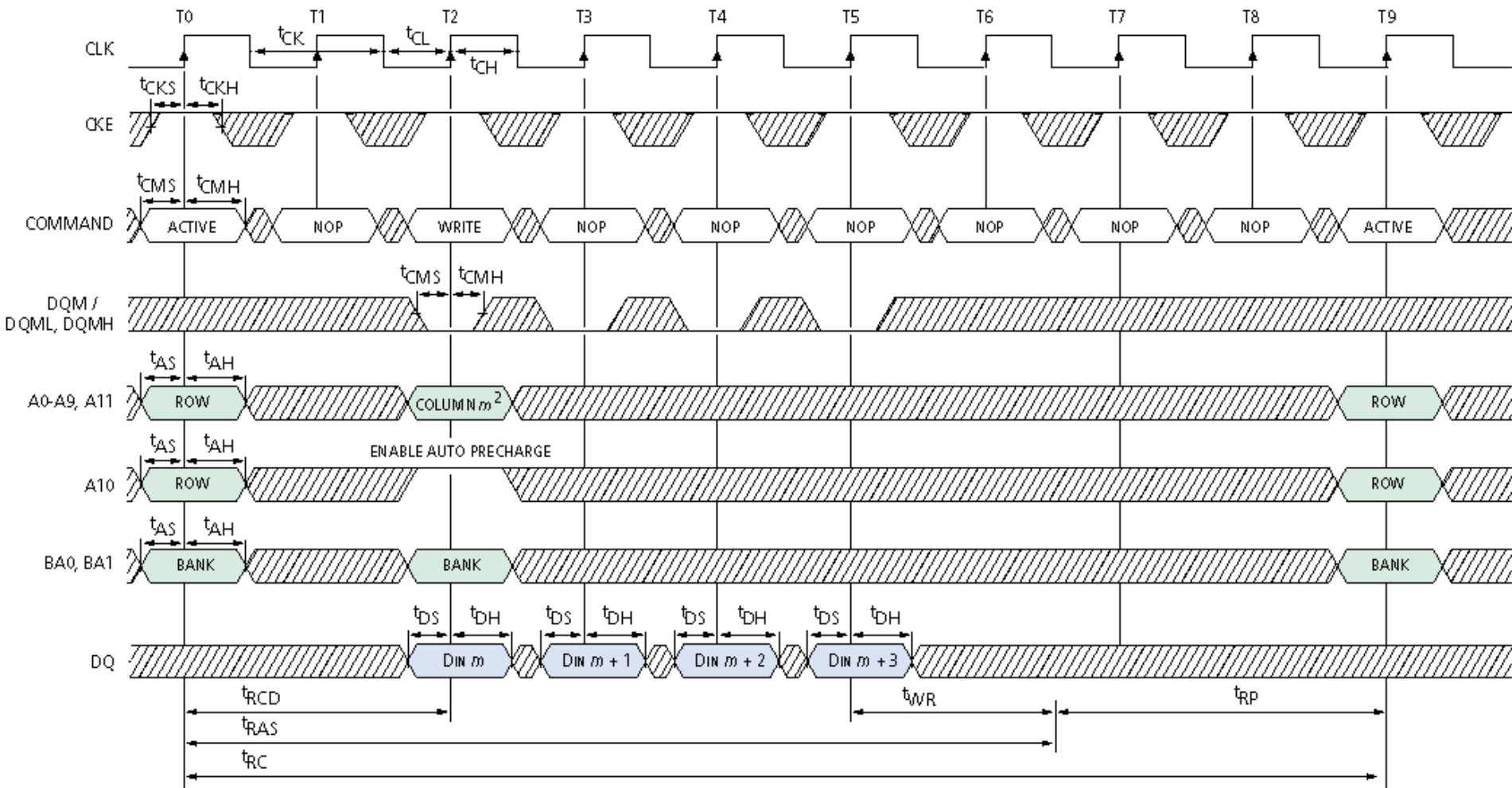


DDR Read Command (with auto precharge)

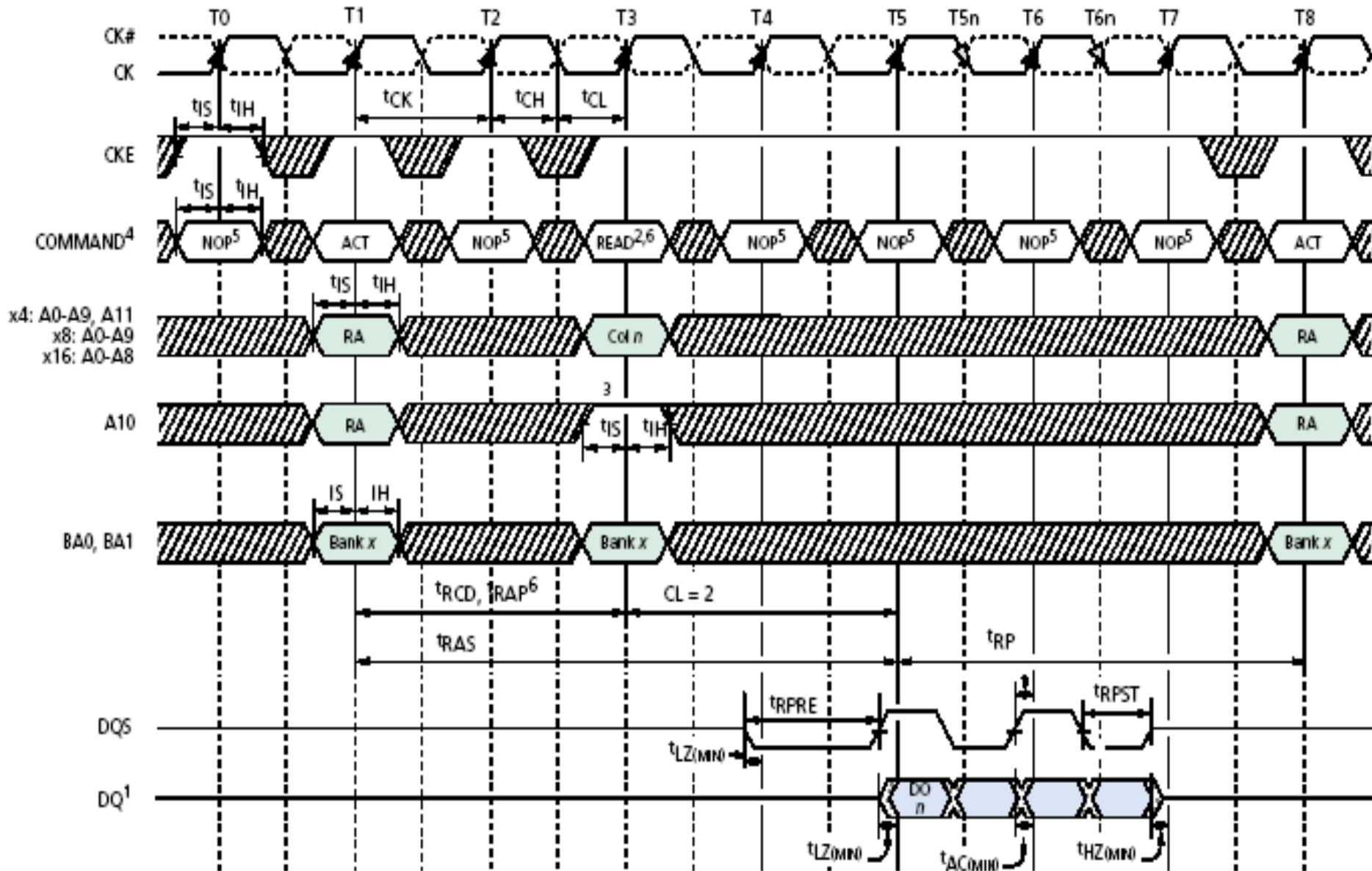

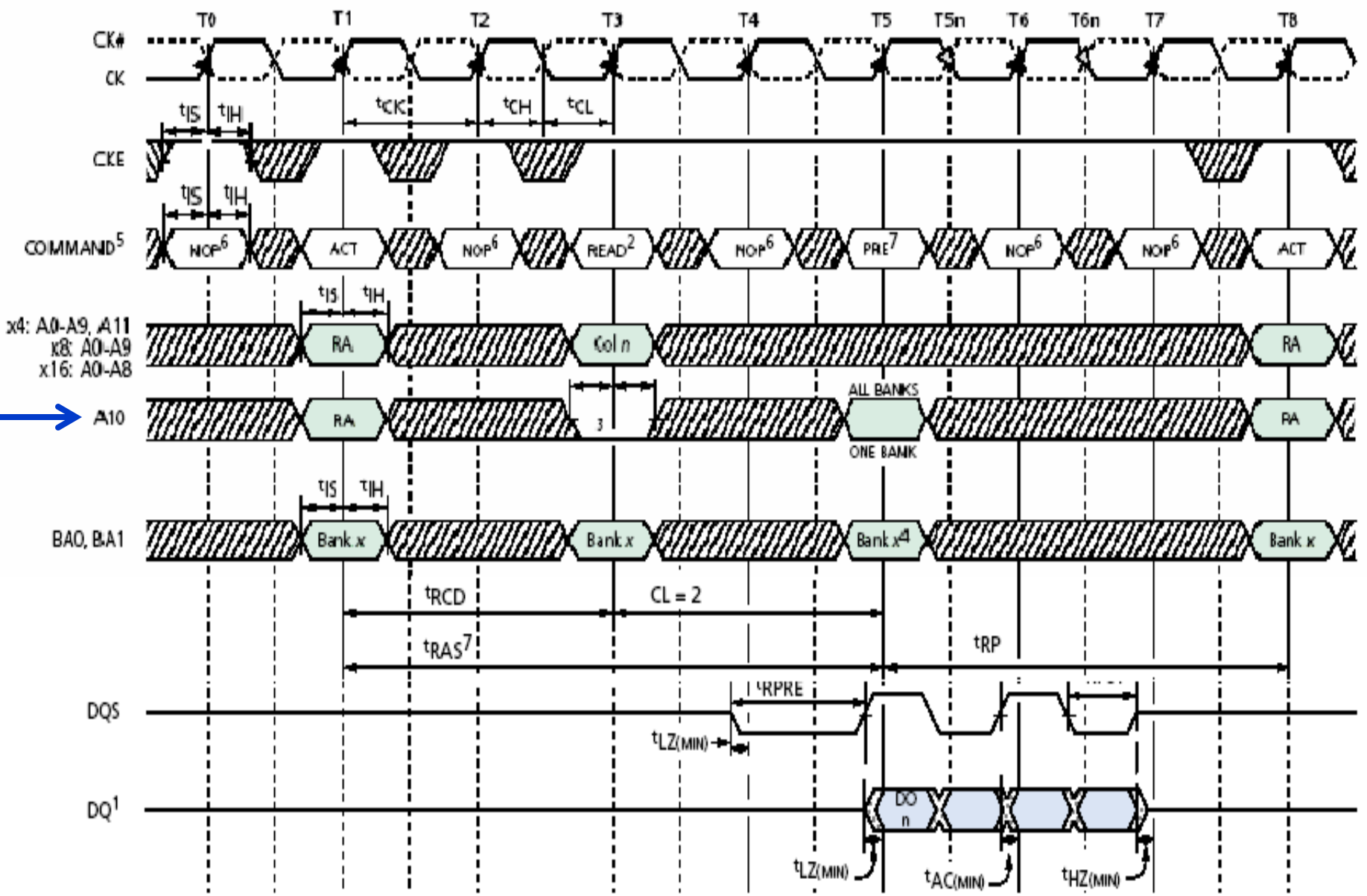DDR Read Command (without auto precharge)




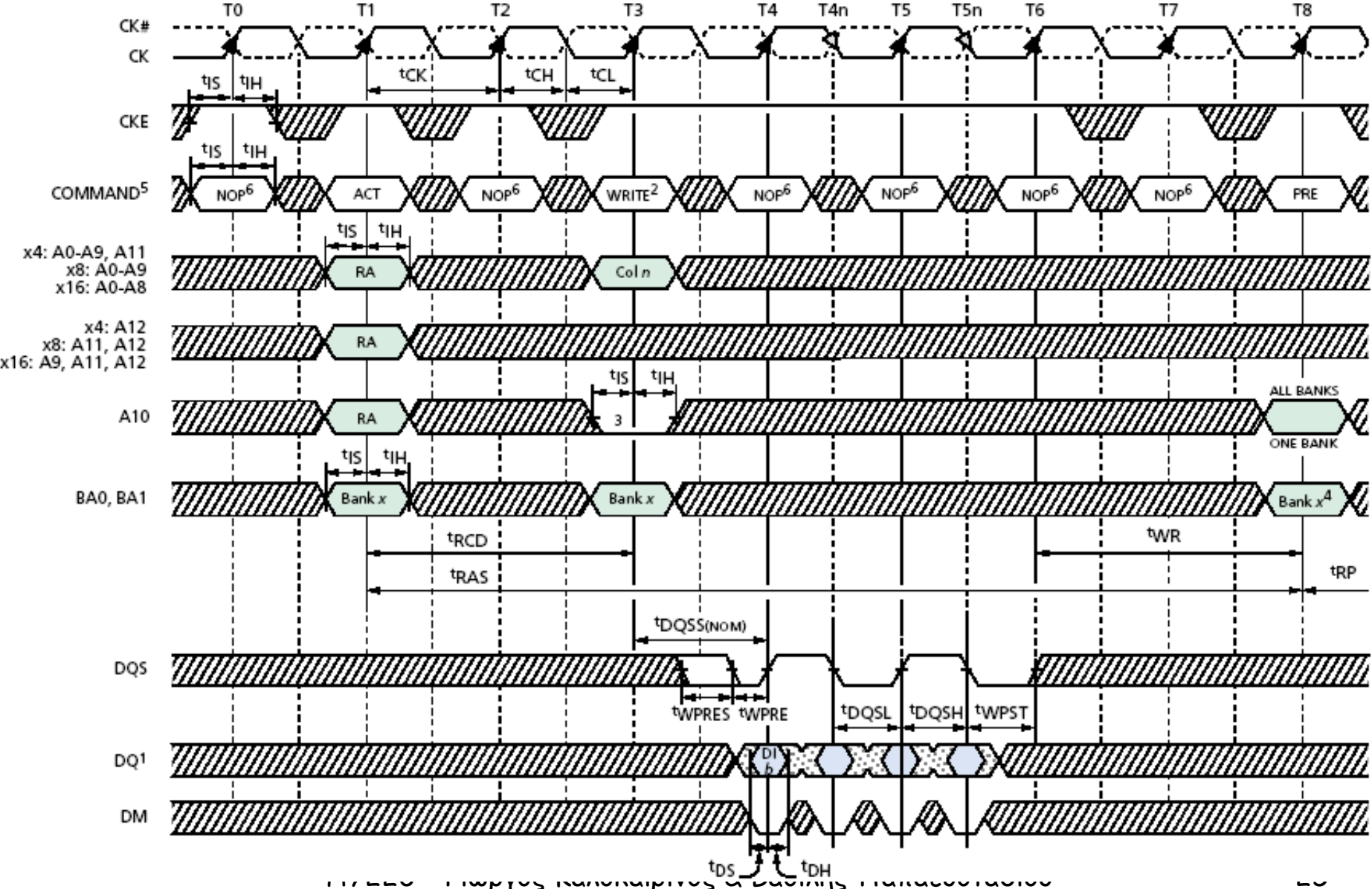DDR Write Command (without auto precharge)



© 2000-2003 Micron Technology, Inc. All rights reserved. Micron, the Micron logo, and the Micron logo with "M" are registered trademarks of Micron Technology, Inc.


DDR: Read - Burst Stop - Write

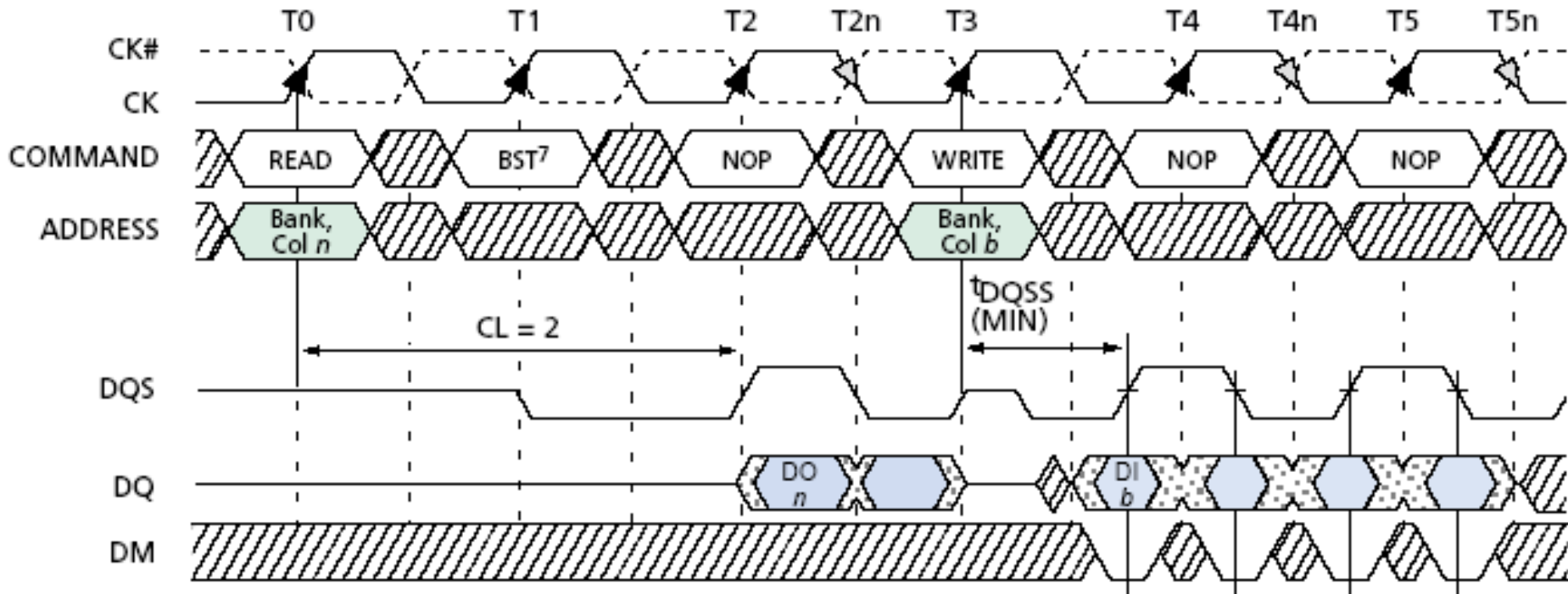

Volatle Memory Comparison


The primary difference between different memory types is the bit cell.

• SRAM Cell

 

- Larger cell \Rightarrow lower density, higher cost/bit
- No dissipation
- Read non-destructive
- No refresh required
- Simple read \Rightarrow faster access
- Standard IC process \Rightarrow natural for integration with logic

• DRAM Cell

 

- Smaller cell \Rightarrow higher density, lower cost/bit
- Needs periodic refresh, and refresh after read
- Complex read \Rightarrow longer access time
- Special IC process \Rightarrow difficult to integrate with logic circuits
- Density impacts addressing