

# Dual-Phase, Dual-Rail Monotonic Circuits

HY590-20


3

## Motivation


- EDA technology delay estimation is becoming unrealistic.
  - STA is unrealistic
    - Wc. Vs. typ.
    - IR drop and crosstalk not taken into account.
    - Variability
  - Clocking overhead
    - Skew
    - Pipeline stage balancing




## Dual-Rail Implementations

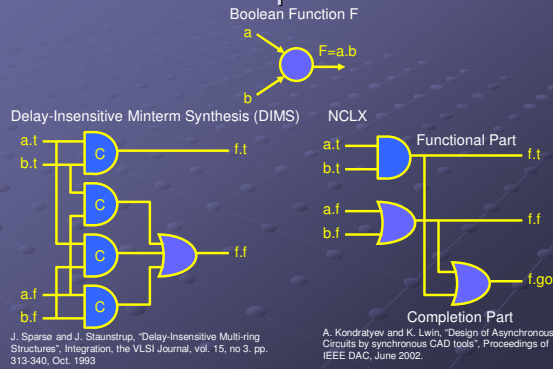

## Our Circuit Universe

 

## Hazards in Combinational Logic

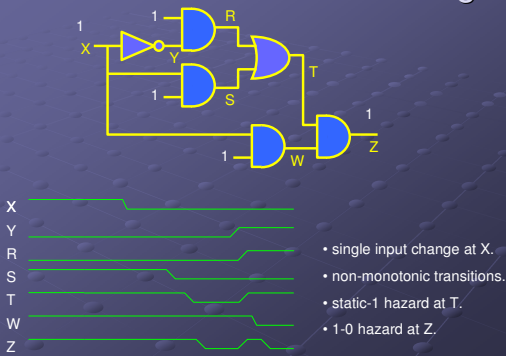


## Monotonicity

- Monotonic Input Transition (MIT):
  - Subset of inputs change  $0 \rightarrow 1$  or  $1 \rightarrow 0$ .
- Monotonic Operation Mode (MOM):
  - Divide circuit operation into **two** MIT phases:
    - (a) subset of inputs changes.
    - (b) subset of outputs changes.
- Dual Rail:
  - (a) and (b) sub-phases where  $\frac{1}{2}$  signals rise/fall.

## MBNs (Monotonic Boolean Networks)


- Unate Functions:
  - $f$  is *increasing (decreasing)* in variable  $x_i$ ;
    - $x_i: 0 \rightarrow 1$ ,  $f$  **cannot change**  $1 \rightarrow 0$  ( $0 \rightarrow 1$ ).
    - $f$  unate in  $x_i$ , iff  $f$  is increasing or decreasing in  $x_i$ .
- Node  $n_i$  with local function  $f_i$  is **+ve**:
  - $x_i$  is +ve and  $f_i$  is *increasing* in  $x_i$ , OR
  - $x_i$  is -ve and  $f_i$  is *decreasing* in  $x_i$ .
- Node  $n_i$  with local function  $f_i$  is **-ve**:
  - $x_i$  is -ve and  $f_i$  is *increasing* in  $x_i$ , OR
  - $x_i$  is +ve and  $f_i$  is *decreasing* in  $x_i$ .
- A node is **monotonic** if it is **either +ve or -ve**.
- A BN is MBN if all its nodes are monotonic.
- MBN is **hazard-free** under **monotonic input transitions**.

## Monotonic Boolean Networks

 

- Assign polarity to every node to check monotonicity.

## Monotonic Boolean Networks

 

## MBN Transformations

- Key Questions:
  - given a BN, how do we transform it to an MBN?
  - given an MBN, which transformations and optimizations can we apply to reduce to another MBN?



## MBN Transformations

- Answers:
  - Provide two transformation procedures, *based on the dual-rail code*, for generating an MBN from a generic BN:
    - Technology-Independent (TI) Conversion
    - Technology-Mapped (TM) Conversion
  - Provide a set of hazard-non-increasing transformations on MBNs.



## TI Conversion

- Steps
  - For each p.i.  $x$ , create  $x^t$  and  $x^f$  representing the true and false evaluations of  $x$ .
  - For each node implementing  $y_i = f_i(x_1, \dots, x_n)$ , create two nodes:
    - $y_i^t = DR(f_i(x_1, \dots, x_n))$  and  $y_i^f = DR(f_i(x_1, \dots, x_n))$
    - $y = 'x$ , special case,  $y^t = x^t$ ,  $y^f = x^f$
  - Define DR recursively (Shannon's exp.):
    - $DR(0) = 0$ ,  $DR(1) = 1$
    - $DR(x.f_x + 'x.f_{x'}) = x^t.DR(f_x) + x^f.DR(f_{x'})$

## TI Conversion

- Conversion Theorem:
  - Given:
    - function  $y = f(x_1, \dots, x_n)$
    - Assumption that  $x^i = x_i^1 = 'x_i^1$
  - It holds that:
    - $y = y^i = 'y^i$
- Proof: by induction on  $x_i$ 
  - $i = 0$ ,  $DR(0) = 0$ ,  $i = 1$ ,  $DR(1) = 0$
  - Split  $y^i$ ,  $y^j$ , for  $i$ , using S.E.,
  - by induction  $DR(f_x^i) = f_x^i$ ,  $DR(f_x^j) = f_x^j$ .

## Shannon's Expansion


- Boolean Relation,  $f: B^m \rightarrow B^n$ :
- Cofactors of  $f$ :
  - for  $f(x_1, x_2, \dots, x_i, \dots, x_n)$ 
    - co-factor w.r.t.  $x_i: f(x_1, x_2, \dots, 1, \dots, x_n)$
    - co-factor w.r.t.  $'x_i: f(x_1, x_2, \dots, 0, \dots, x_n)$
- Shannon's Expansion:
  - Let  $f: B^n \rightarrow B$ :
  - $\Rightarrow f(x_1, x_2, \dots, x_i, \dots, x_n) =$ 
    - $(x_i \cdot f_{x_i}) + ('x_i \cdot f_{'x_i})$  [sum form]
    - $(x_i + f_{x_i}) \cdot ('x_i + f_{'x_i})$  [product form]

## TI Example

- $y = a'b + b(c + 'd)$ 
  - would be converted into:
    - $y^i = DR(a'b + b(c + 'd)) = a^i b^i + b^i(c^i + d^i)$
    - $y^j = DR('a'b + b(c + 'd)) = (a^i + b^i)(b^i + c^i d^i)$
- How do I convert?
  - Use S.E.
  - assume that  $x^i = x_i^1 = 'x_i^1$ , for all  $x$  and  $i$ .
  - Use the SIS **dr package!**


## TI Conversion - #1

- Original BN:

 


## TI Conversion - #2

- Dual-Rail Conversion:

 

## TI Conversion - #3

- Technology Mapping to a library:

 


## TM Conversion

### Steps

- For each gate, producing signal  $y_i^t$ , from signals  $y_j^t, \dots, y_k^t$ , add a *dual* gate, based on De Morgan's law.
- Label each node +ve or -ve, starting from p.o.'s, according to gate polarities. In case of multiple paths, select longest.
- For each gate input or p.i., which is inconsistently labelled, invert and connect to its dual.


## TM Conversion - #1

### Original technology-mapped circuit:

 


## TM Conversion - #2
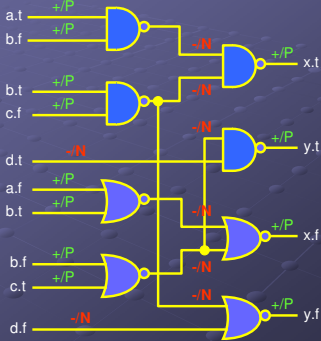
### Dual-Rail Conversion and Level labeling:




## TM Conversion - #2
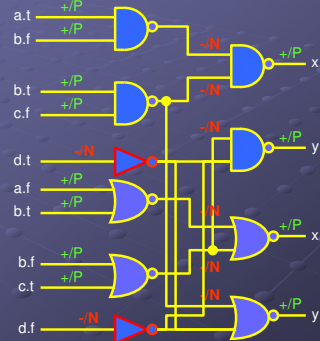
### Phase Correction by inverter introduction:



## TM Conversion - #3
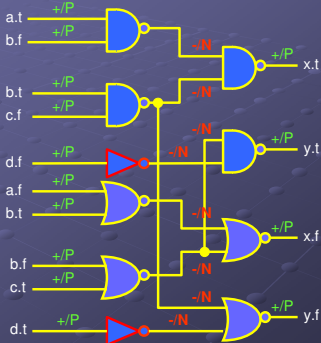
### Phase Correction by inverter introduction:



## MBN Conversion Approaches

- Both TI and TM approaches equivalent !
  - TI: early synthesis stages.
    - Based on recursive Shannon Expansion.
  - TM: mapped and analyzed circuits.
    - Based on De Morgan's Law and phase correction.

## Hazard-non-Increasing Transformations

- Set of transformations that preserve MBN:
  - De Morgan's laws.
  - Dual global and global flow.
  - Tree decomposition.
  - Gate replication.
  - Collapsing.
  - Kernel-factoring.
  - Cube-factoring.




## Fast Reset and CD

- MBN circuit operates at  $\frac{1}{2}$  speed:
  - **WHY?**
  - *all p.i.'s must be reset before the next monotonic phase begin.*
    - in D.R. this is the 00 value for every pair.
- **Fast Reset:**
  - Speed-up reset phase
  - Force more gate outputs to their "quiescent" value.
  - Tradeoff: number of gates reset v.s. capacitance of reset signal.


## MBN Flows

- **Flow 1**
  - TM-conversion using AWK scripts.
  - Fanout-fixing in Synopsys DC (max\_delay).
- **Flow 2**
  - TI-conversion using SIS dr package.
  - Optimization in Synopsys DC (hazards?).
- **Flow 3**
  - TM-conversion using AWK scripts.
  - Optimization in Synopsys DC (hazards?).
- Run them on SIS Benchmarks + RTL Examples (DLX and DES).


## Results – Scatter #1

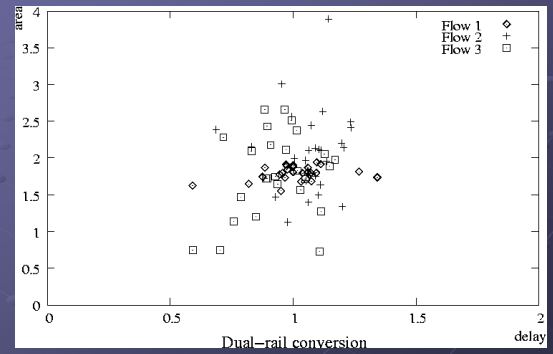

## Results – Scatter #2

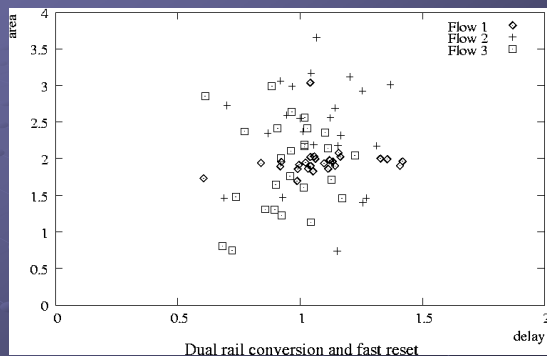


## Results – Scatter #3

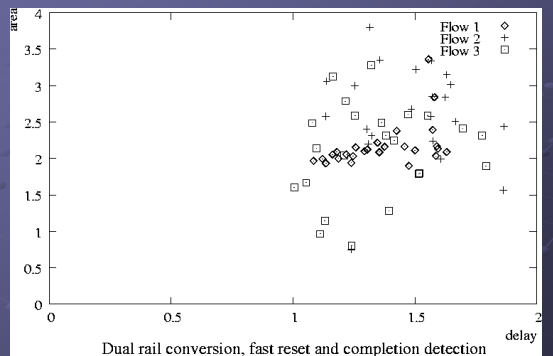

## Use Cases

- C.L. with CD can be used in two environments:
  - Synchronous or Asynchronous.
  - Delay Fault Testing for Free (for MBN).
- Synchronous environment
  - use CD to check completion w.r.t. clock.
  - produce *synchronization error* signal if CD signal transitions after the clock edge.
  - Error signal:
    - Bin chips according to performance
    - provide on-line testing capability
- Asynchronous environment
  - performance

## Use Cases

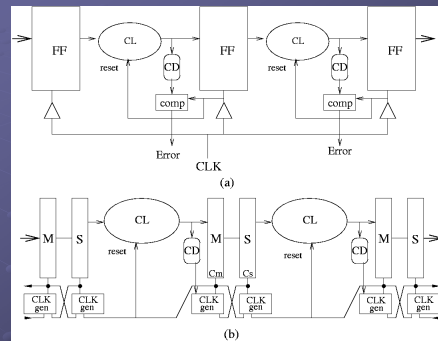

## Conclusions

- Using MBNs we can design **FAST, static CMOS**, Monotonic circuits!
- Fast DR + De-synchronization:
  - COMPLETE design flow for asynchronous circuits!
  - C.L. handled by Fast DR (partially).
  - F.F./Lat. handled by De-synchronization.
- Variability:
  - Asynchronous OR synchronous with error detection (and correction?).
  - Delay Fault Testing!