

HY 590.20

Χρονισμός Ψηφιακών Συστημάτων Χρήστος Σωτηρίου

7

1

Control Circuits

- Many methods, tools, assumptions, frameworks
- Balsa generated both control and data-path
- We now consider one method / tool for control-only spec, verification and synthesis:
 - Assumption: Speed independent control for speed independent bundled data
 - Method: Signal Transition Graph
 - A special type of Petri net : FC-PTnet
 - Tool: **Petrify** (mostly from Jordi Cortadella at UPC)

2


Delay Models

- Fixed delay: $d=c$
- Min-max delay: choose $d \in [m, M]$
 - Max delay: $d \in [0, M]$
 - Low-bounded delay: $d \in [m, \infty)$
- Unbounded delay: $d \in [0, \infty)$

- Inertial delay: Glitches are filtered.
 - We don't assume inertial delays in async control design


3

Petri net, Signal Transition Graph (STG)

 

4

Separating Inputs, Outputs and Internals

 

5


In the STG:

- PN transition are signal transitions
- PN places and arcs are causal relations
- Simple places (one arc in, one arc out) are omitted
- MARKING
 - ≡ assignment of tokens to places
 - ≡ state of the circuit

6

Token Preservation (from Lecture #1)

 
- Tokens do not disappear
- Tokens do not appear (from nowhere)
- One token does not overtake another
- A transition with n inputs and m outputs:
 - waits for n tokens on inputs
 - Generates m tokens on outputs



7

State Graph (SG)


State: `abc`

 

- SG more complex than STG
- Bad for design spec
- Needed for synthesis


8

State Graph (SG)

 

9

State Graph (SG)

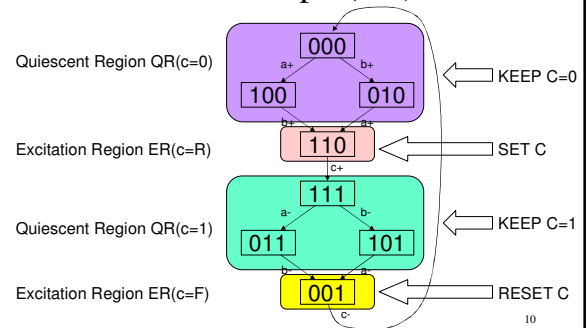


10

Synthesis: C Element

- Two methods:
 - Using gates
 - Using SR latch


11

Synthesis: C Element using gates

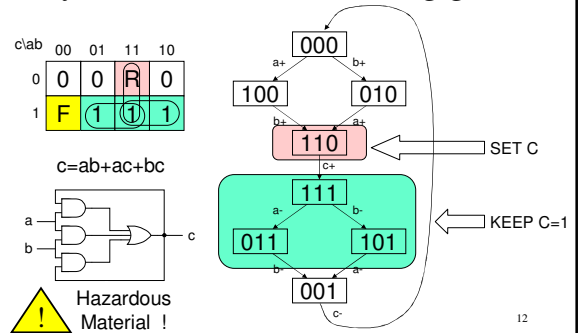

12

Hazardous Conditions

 


13

Hazardous Conditions

- Hazards are not an issue in sync circuits
- **Hazards can be deadly in (some) async circuits**
- We **can** build hazard-free circuits
- We can impose timing assumptions and add delays

14


Hiding Hazards Behind Delays

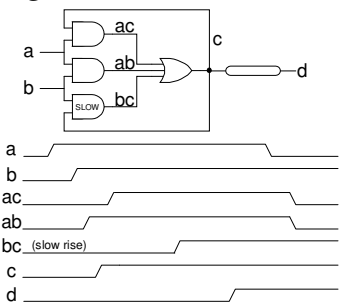

Do you like slowing your circuit ?

15

Avoiding Hazards with Complex Gates

 


•Theoretically, same hazard problem (e.g. T1 slow)

•Must use caution or delay output

16

Synthesis: C Element using SR Latch

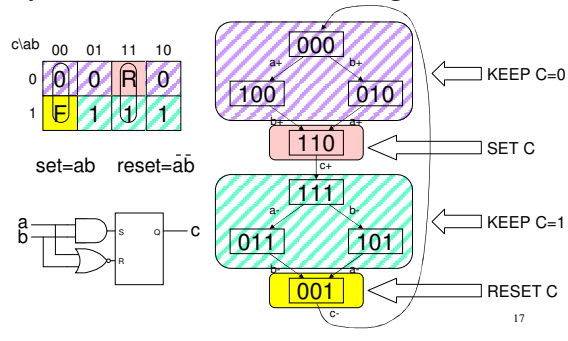


17

Synthesis using SR latches

- Needs SET, RESET regions
- May use KEEP 0, KEEP 1 regions
- May use unreachable states (more later...)
- Area / performance / power may be more or less than gate circuits
- May use C elements instead of SR latches
- SR latches enable implementation with standard libraries


18

 Implementation using Latches or C elements




19

Generalized C Element

 


20

More interesting PNs and STGs

 


21

STG with Input Choice

 


22

A "Simple" Choice Net

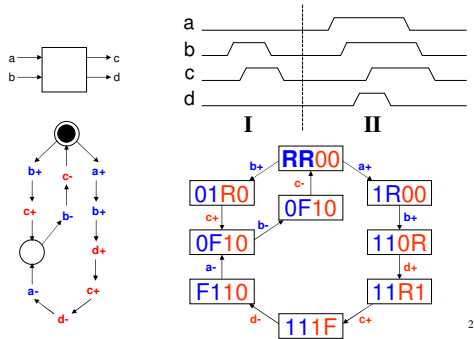

23

Unreachable States

 

24

Regions and Maps

For c

cd\ab	00	01	11	10
00	0 R 0 0			
01	x x R x			
11	x x 1 x			
10	F 1 1 x			

$c = d + a'b + bc$
 $\text{set}(c) = d + a'b$
 $\text{reset}(c) = b'$

25

$c = d + a'b + bc$

$\text{set}(c) = d + a'b$
 $\text{reset}(c) = b'$

26

Regions and Maps

For d

cd\ab	00	01	11	10
00	0 0 R 0			
01	x x 1 x			
11	x x F x			
10	0 0 0 x			

$d = abc'$
 $\text{set}(d) = abc'$
 $\text{reset}(d) = c$

27

Walks on SG and KM

cd\ab	00	01	11	10
00	x x x x			
01	x x x x			
11	x x x x			
10	x x x x			

I II

A decomposed gate implementation is not speed-independent due to hazards. Explain, using the walks.

28

STG Rules

- Any STG:
 - Input free-choice—Only mux inputs may control the choice)
 - 1-Bounded—Maximum 1 token per place
 - Liveness—No deadlocks
- STGs for Speed Independent circuits:
 - **Consistent state assignment**
 - Signals strictly alternate between + and -
 - **Persistency**
 - Excited signals fire, namely they cannot be disabled by another transition
- Synthesizable STG:
 - **Complete state coding or Unique state coding**
 - Different markings must represent different states (USC), or
 - CSC + separation of next state by environment signals


29

• We use the following circuit to explain STG rules:

30

1-Bounded (Safety)

 - STG is *safe* if no place or arc can ever contain more than one token
- Often caused by one-sided dependency



STG is not safe:


If left cycle goes fast and right cycle lags,
then arc $ack+ \rightarrow REQ+$ accumulates tokens.
($REQ+$ depends on both $ack+$ and $ACK-$)

Possible solution: stop left cycle by right cycle - - - ->

31

Liveness

 - STG is *live* if from every reachable marking, every transition can eventually be fired




- The STG is not live:
 - Transitions $reset$, $reset_ok$ cannot be repeated.
- But non-liveness is useful for initialization

32

Consistent State Assignment

 
- The following subset of STG makes no sense:



33

Persistence

 - STG is *persistent* if for all arcs $a^* \rightarrow b^*$, other arcs ensure that b^* fires before opposite transition of a^* (* is either + or -)
- Non-persistence may be caused by one-sided relations



STG is not persistent (in addition to being unsafe):

If left cycle goes fast and right cycle lags,
then $ack+ \rightarrow ack-$ before $REQ+$.

Danger: Logic design may be $REQ+ = ack+$

Exception: If $a^* \rightarrow b^*$, assume that the environment assures persistency.



Possible solution: stop left cycle by right cycle. - - - ->

34

Complete State Coding

- STG has a *complete state coding* if no two different markings have identical values for all signals.

req,ack,REQ,ACK:

  


35

Complete State Coding

- Possible solution: Add an internal state variable


req,ack,REQ,ACK,x:

 

36

A faster STG?

- Does it need an extra variable?

 

37