


HY 590.20

Χρονισμός Ψηφιακών Συστημάτων
Χρήστος Σωτηρίου
8

1


A faster STG?

- Does it need an extra variable?

 

2

Drawn by draw_astg

 


Note reverse colors

INPUTS: r,A
OUTPUTS: aR

3

The SG


req,ack,REQ,ACK:

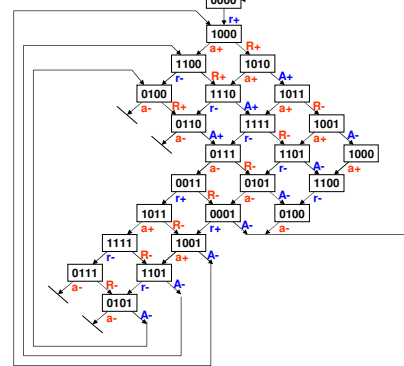

4


The SG

req,ack,REQ,ACK:

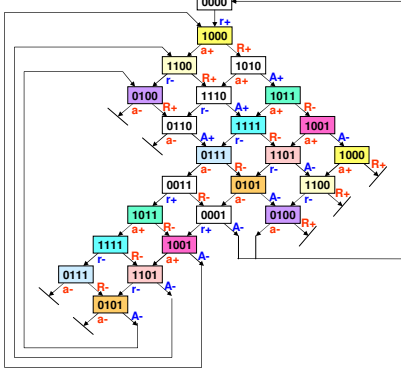


5

Drawn by write_sg & draw_astg

 


6

Extra states inserted by petrify

 

7


Rearranged STG

 

Initial Internal State: $c0=c1=c2=1$

8

The new State Graph...

 

9

The Synthesized Complex Gates Circuit

```

INORDER = r A a R csc0 csc1 csc2;
OUTORDER = [a] [R] [csc0] [csc1] [csc2];
[a] = a (csc2 + csc0) + csc1';
[R] = csc2 (csc0 (a + r) + R);
[csc0] = csc0 (csc1' + a') + R' csc2;
[csc1] = r' (csc0 + csc1);
[csc2] = A' (csc0' (csc1' + a') + csc2);
    
```

10

Technology Mapping

```

INORDER = r A a R csc0 csc1 csc2;
OUTORDER = [a] [R] [csc0] [csc1] [csc2];
[0] = R'; # gate inv: combinational
[1] = [0]' A' + csc2'; # gate oai12: combinational
[a] = a csc0' + [1]; # gate sr_nor: asynch
[3] = csc1'; # gate inv: combinational
[4] = csc0' csc2' [3]'; # gate nor3: combinational
[5] = [4]' (csc1' + R'); # gate aoi12: combinational
[R] = [5]'; # gate inv: combinational
[7] = (csc2' + a') (csc0' + A'); # gate aoi22: combinational
[8] = csc0'; # gate inv: combinational
[csc0] = [8]' csc1' + [7]'; # gate oai12: combinational
[csc1] = A' (csc0 + csc1); # gate rs_nor: asynch
[11] = R'; # gate inv: combinational
[12] = csc0' ([11]' + csc1'); # gate aoi12: combinational
[csc2] = [12] (r' + csc2) + r' csc2; # gate c_element1: asynch
    
```

11


The Synthesized Gen-C Circuit

```

INORDER = r A a R csc0 csc1 csc2;
OUTORDER = [a] [R] [csc0] [csc1] [csc2];
[0] = csc0' csc1 (R' + A);
[1] = csc0 csc2 (a + r);
[2] = csc2' A;
[R] = R [2]' + [1]; # mappable onto gC
[4] = a csc1 csc2';
[csc0] = csc0 [4]' + csc2; # mappable onto gC
[6] = r' csc0;
[csc1] = csc1 r' + [6]; # mappable onto gC
[8] = A' csc0' (csc1' + a');
[csc2] = csc2 R' + [8]; # mappable onto gC
[a] = a [0]' + csc1'; # mappable onto gC
    
```

12

Petrify Environment

 


13

Petrify

- Unix (Linux) command line tool
- **petrify -h** for help (flags etc.)
- **petrify -cg** for complex gates
- **petrify -gc** for generalized C-elements
- **petrify -tm** for tech mapping
- **draw_astg** to draw
- **write_sg** to create state graphs
- Documented on line, incl. tutorial
 - See /usr/local_linux/async/doc/petrify


14

A safer STG?

 


15

A safer STG?

 


16

The safer STG is a serial circuit

 


17

Yet another STG?

 


18

Yet another STG?

 


19

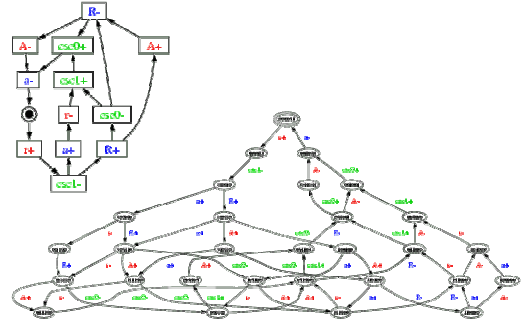


20

Output Handshake First

 

21

Still a serial controller

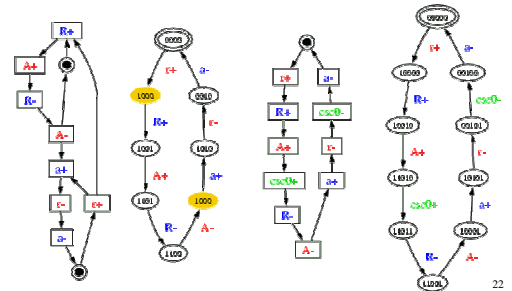


22

Synthesis


```

 INORDER = r A a R csc0;
OUTORDER = [a] [R] [csc0];
[a] = csc0 A';           # gate and2_1: combinational
[R] = r csc0';          # gate and2_1: combinational
[2] = A' (csc0' + r');  # gate aoi12: combinational
[csc0] = [2]';         # gate inv: combinational
    
```




23

A different STG

 

24

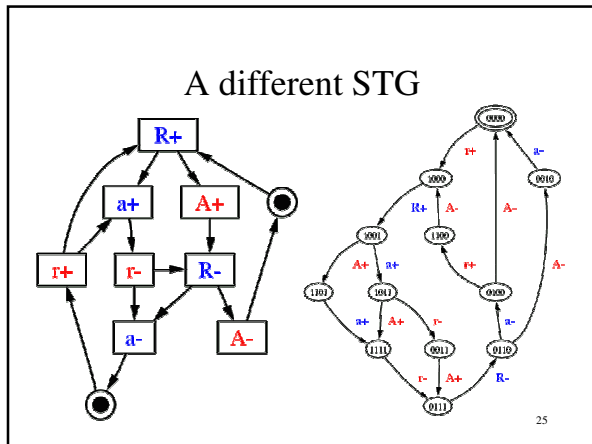


Synthesis



```

INORDER = r A a R;
OUTORDER = [a] [R];
[a] = R;
[1] = r A';
[2] = r' A;
[R] = R [2]' + [1]; # mappable onto qC
→R = R(Ar')' + A'r = R(A'+r) + A'r = A'r + RA' + Rx
  
```


26

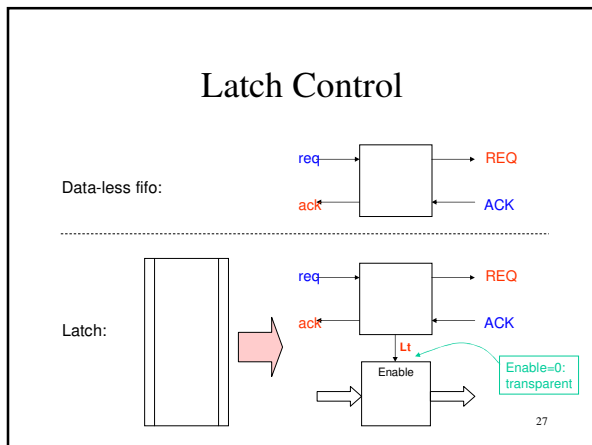

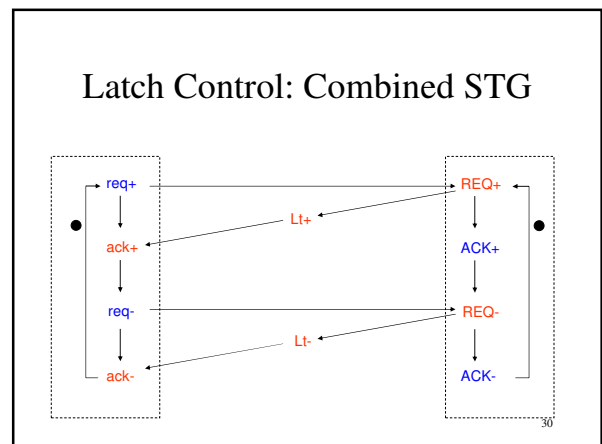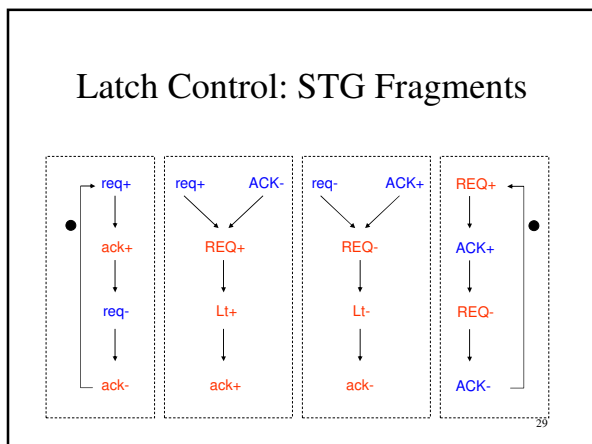
- ### Constraints on sequence of events
- Must keep input data available until after it is latched
 - Assume input data available only when req=1
 - Once ack+, req- (and input data invalid) can follow very fast
 - Lt+ before ack+
- 28



Latch Control: Combined STG

 


31

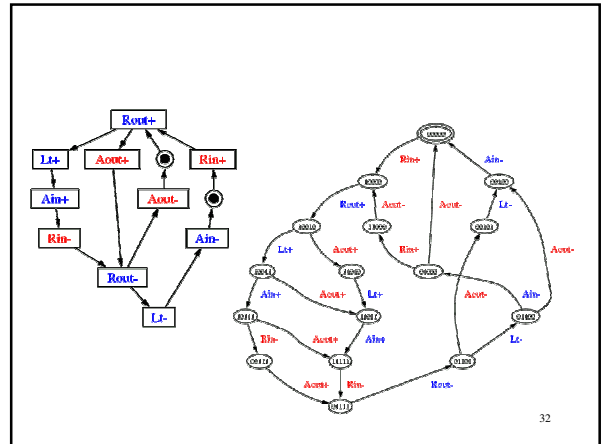

32

```

 
INORDER = Rin Aout Ain Rout Lt;
OUTORDER = [Ain] [Rout] [Lt];
[Ain] = Lt;
[1] = Aout' Rin;
[2] = Aout Rin';
[Rout] = Rout [2]' + [1]; # mappable onto gc
[Lt] = Rout;
→ R = R(Ax') + A'x = R(A'+x) + A'x = A'x + RA' + Rx
    
```



33

MUX Control

 
- So far all examples are doable “by hand”
- A deceptively simple example:
Control for 4-phase bundled data mux



34

4-phase Bundled-data Mux

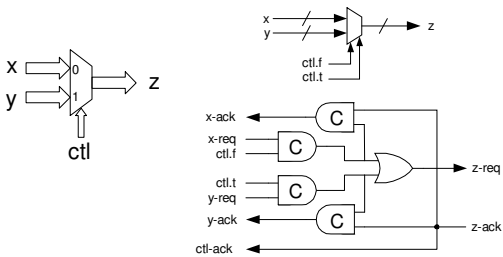- We have already drawn this (dual-rail control):




Easier to start with the dual-rail control

35

The environment

 - Four *independent* environments (rCf, rCt share aC)
- Must not specify any dependency by mistake:




36

The control


- A+ must precede a0+ or a1+ (make sure data passed through and were captured)
- In0 and In1 handshakes must be made MUTEX
- Choices are matches with Merges

37

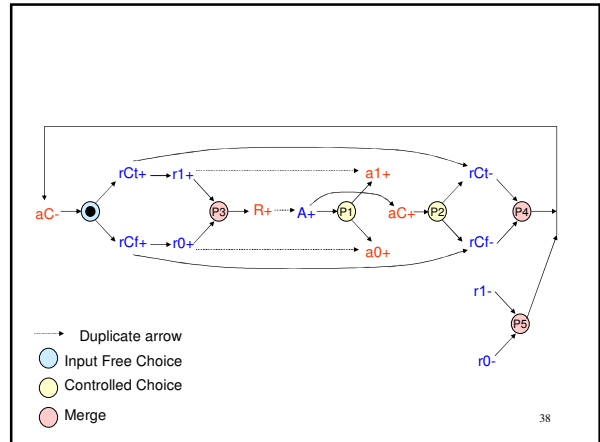

38


mux.g

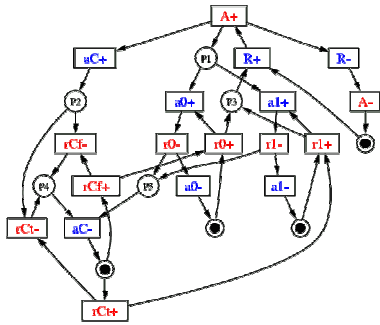

39


mux.gc

 - Replicated transitions: R+, R+/1
- Inserted state variable to retain In0 vs. In1 info



40

Compact state graph

 

41


Mux Control Synthesis

```

INORDER = r0 r1 rCf rCt A a0 a1 aC R csc0 csc1;
OUTORDER = [a0] [a1] [aC] [R] [csc0] [csc1];
[0] = r0 csc0;
[a1] = csc1 r1;
[2] = csc1 (A + csc0);
[3] = rCt' rCf' csc1';
[aC] = aC [3]' + [2]; # mappable onto gC
[R] = a0' csc0' csc1 r0 + csc0 csc1';
[6] = a0' csc1 A r0 + csc1' r1 A';
[7] = aC (r0' + a0);
[csc0] = csc0 [7]' + [6]; # mappable onto gC
[9] = r0 A' + csc0 A;
[10] = r0' csc0' r1';
[csc1] = csc1 [10]' + [9]; # mappable onto gC
[a0] = a0 r0 + [0]; # mappable onto gC
  
```


42

Another Mux (4p ctl, bd) (Fig 6.24)

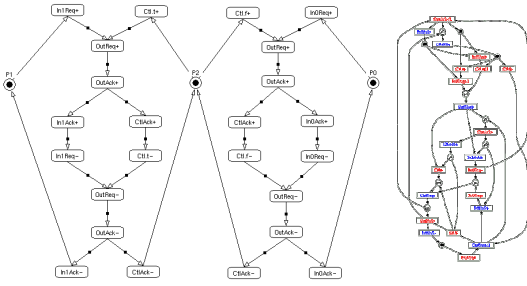


43

SG for the Fig 6.24 mux

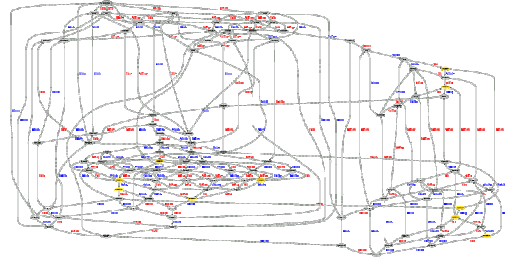

44

All-bundled Mux

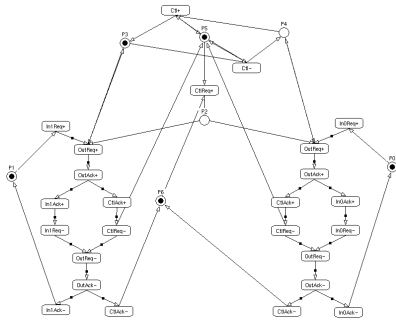

45


All-bundled Mux Synthesis

```

INORDER = In0Req OutAck In1Req Ctl1 Ctl1Req In1Ack In0Ack OutReq
          Ctl1Ack csc0;
OUTORDER = [In1Ack] [In0Ack] [OutReq] [Ctl1Ack] [csc0];
[In1Ack] = OutAck csc0';
[In0Ack] = OutAck csc0;
[2] = Ctl1Req (In1Req csc0' + In0Req Ctl1');
[3] = Ctl1Req' (In1Req' csc0' + In0Req' csc0);
[OutReq] = OutReq [3]' + [2]; # mappable onto gC
[5] = OutAck' csc0;
[Ctl1Ack] = Ctl1Ack [5]' + OutAck; # mappable onto gC
[7] = OutAck' Ctl1Req';
[8] = Ctl1Req Ctl1;
[csc0] = csc0 [8]' + [7]; # mappable onto gC
    
```

46

Reduced concurrency mux

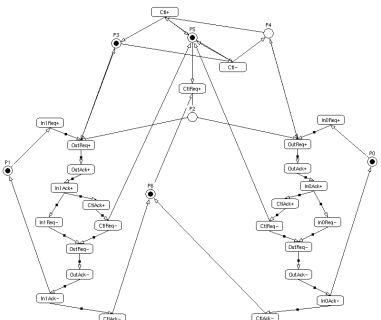


47

Following slides borrowed from Jordi Cortadella, UPC

A simple filter: specification


```

 y := 0;
loop
  x := READ (IN);
  WRITE (OUT, (x+y)/2);
  y := x;
end loop
    
```



48



A simple filter: block diagram

 

- x and y are level-sensitive latches (transparent when $R=1$)
- $+$ is a bundled-data adder (matched delay between R_a and A_a)
- R_{in} indicates the validity of IN
- After $A_{in}+$ the environment is allowed to change IN
- $(R_{out}A_{out})$ control a level-sensitive latch at the output



49

A simple filter: control spec.

  



50

A simple filter: control impl.

  

51

Control: observable behavior

  

52